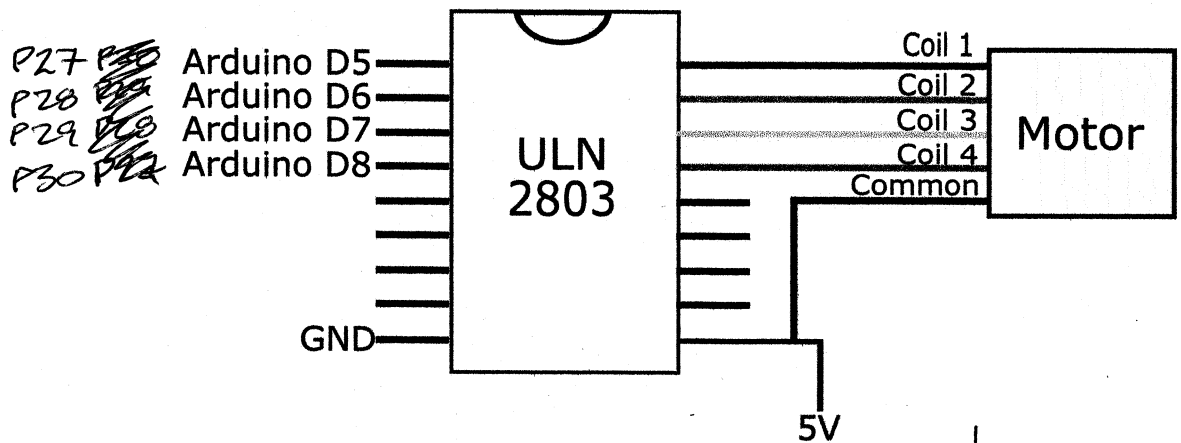


## 1.2 ULN2803 IC:




ULN2803 is a high current, high voltage IC, used to drive high power loads upto 500mA/50V such as relays, motors etc.



## 2. Hardware required

S.No.	Item	Quantity
1	Arduino UNO	1
2	Breadboard	1
3	28BYJ-48 Stepper Motor	2
4	ULN2803 IC	7
5	Male to male Jumper	11

E/A 4089  
Neo Board

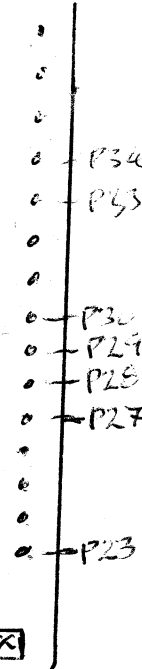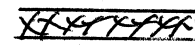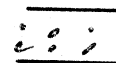

## 3. Connection:

<del>P26</del>		MOTOR	ULN2803
P27	P1.6	Coil 1	1B
P28	P1.5	Coil 2	2B
P29	P1.3	Coil 3	3B
P30	P1.2	Coil 4	4B

MIROBOT STEPPER BOARD:

